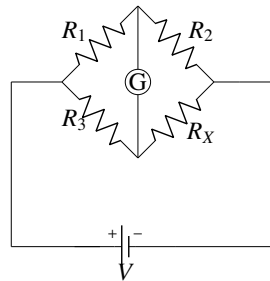



# 2015-EE-''14-26''

ai24btech11028 - Ronit Ranjan


- 1) Consider a function  $\vec{f} = \frac{1}{r^2} \hat{r}$ , where  $r$  is the distance from the origin and  $\hat{r}$  is the unit vector in the radial direction. The divergence of this function over a sphere of radius  $R$ , which includes the origin is [2015-EE]
- 0
  - $2\pi$
  - $4\pi$
  - $R\pi$
- 2) When the wheatstone bridge shown in the figure is used to find the value of resistor  $R_X$ , the galvanometer  $G$  indicates zero current when  $R_1 = 50\Omega$ ,  $R_2 = 65\Omega$  and  $R_3 = 100\Omega$ . If  $R_3$  is known with  $\pm 5\%$  tolerance on its nominal value of  $100\Omega$ , what is the range of  $R_X$  in Ohms? [2015-EE]



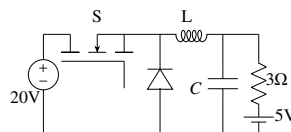
- [123.50, 136.50]
  - [125.89, 134.12]
  - [117.00, 143.00]
  - [120.25, 139.75]
- 3) A (0 – 50A) moving coil ammeter has a voltage drop of 0.1V across its terminals at full scale deflection. The external shunt resistance (in milliohms) needed to extend its range to (0-500 A) is [2015-EE]
- 4) Of the four characteristics given below, which are the major requirements for an instrumentation amplifier? [2015-EE] P. High common mode rejection ratio Q. High input impedance R. High linearity S. High output impedance
- P, Q and R only
  - P and R only
  - P, Q and S only
  - Q, R and S only
- 5) In the following chopper, the duty ratio of switch  $S$  is 0.4. If the inductor and capacitor are sufficiently large to ensure continuous inductor current and ripple free capacitor voltage, the changing current (in Ampere) of the 5V battery, under steady-state, is \_\_\_\_\_ [2015-EE]



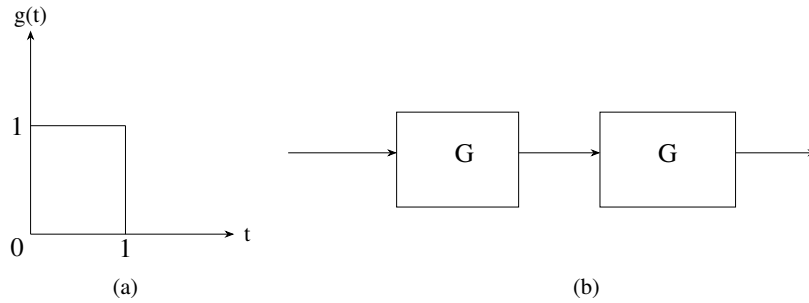
- 6) A moving average function is given by  $y(t) = \frac{1}{T} \int_{t-T}^t u(\tau) d\tau$ . If the input  $u$  is a sinusoidal signal of frequency  $\frac{1}{2T}$  Hz, then in steady state, the output  $y$  will lag  $u$  (in degree) by \_\_\_\_\_ [2015-EE]
- 7) The impulse response  $g(t)$  of a system,  $G$ , is as shown in Figure(a). What is the maximum value attained by the impulse response of two cascaded blocks of  $G$  as shown in Figure(b) [2015-EE]



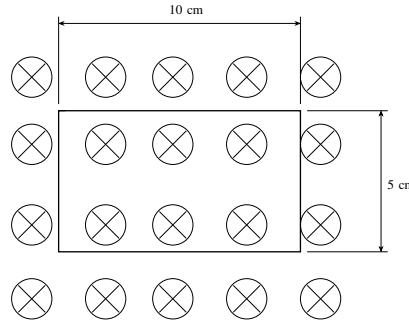- a)  $\frac{2}{3}$   
b)  $\frac{4}{3}$   
c)  $\frac{4}{5}$   
d) 1
- 8) Consider a one-turn rectangular loop of wire placed in a uniform magnetic field as shown in the figure. The plane of the loop is perpendicular to the field lines. The resistance of the loop is  $0.4\Omega$ , and its inductance negligible. The magnetic flux density(in Tesla) is a function of time and is given by  $B(t) = 0.25\sin\omega t$ , where  $\omega = 2\pi \times 50$  radian/second. The power absorbed (in Wat) by the loop from the magnetic field is [2015-EE]



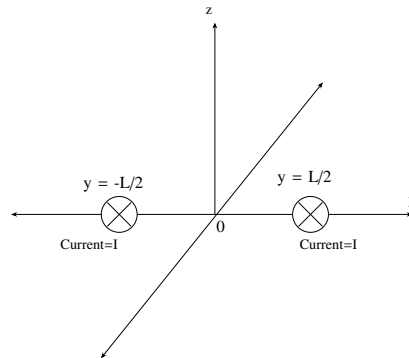
- 9) A steady current  $I$  is flowing in  $-x$  direction through each of the two infinitely long wires at  $y = \pm \frac{L}{2}$  as shown in the figure. The permeability of the medium is  $\mu_0$ . The  $\vec{B}$ - field at  $(0, L, 0)$  is [2015-EE]



- a)  $-\frac{4\mu_0 I}{3\pi L} \hat{z}$   
b)  $+\frac{4\mu_0 I}{3\pi L} \hat{z}$


- c) 0  
d)  $-\frac{3\mu_0 I}{4\pi L} \hat{Z}$

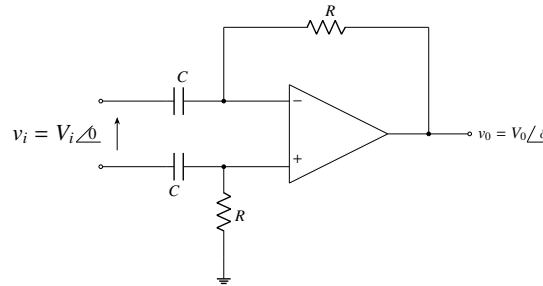- 10) Consider the circuit shown in the figure. In this circuit  $R = 1k\Omega$  and  $C = 1\mu F$ . The input voltage is sinusoidal with a frequency of 5-Hz, represented as a phasor with magnitude  $V_i$  and phase angle 0 radian as shown in the figure. The output voltage is represented as phasor with magnitude  $V_0$  and phase angle  $\delta$  radian. What is the value of the output phase angle  $\delta$ (in radian) relative to the phase angle of the input voltage? [2015-EE]




- a) 0  
b)  $\pi$   
c)  $\frac{\pi}{2}$   
d)  $-\frac{\pi}{2}$

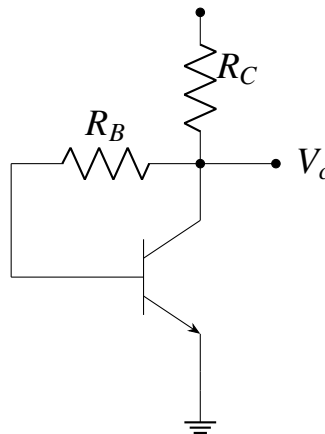- 11) In the given circuit, the silicon transistor has  $\beta = 75$  and a collector voltage  $V_C = 9V$ . Then the ratio of  $R_B$  and  $R_C$  is \_\_\_\_\_. [2015-EE]



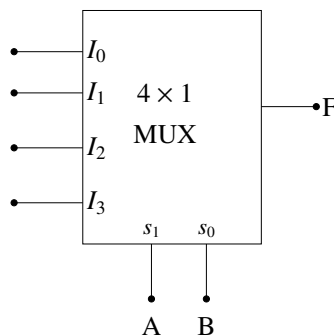
- 12) In the  $4 \times 1$ , the output F is given by  $F = A \oplus B$ . Find the required input  $I_3 I_2 I_1 I_0'$  [2015-EE]



- a) 1010

- b) 0110
- c) 1000
- d) 1110

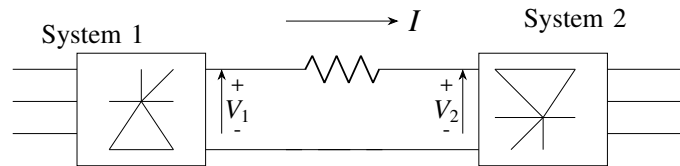13) Consider a HVDC link which used thyristor based line-commutated converters as shown in the figure. For a power flow of 750 MW from a System 1 to System 2, the voltage at the two ends, and the current, are given by :  $V_1 = 500kV$ ,  $V_2 = 485kV$  and  $I = 1.5kA$ . If the direction of power flow is to be reversed(that is, from System 2 to System 1) without changing the electrical connections, then which one of the following combinations is feasible? [2015-EE]



- a)  $V_1 = -500kV$ ,  $V_2 = -485kV$  and  $I = 1.5kA$
- b)  $V_1 = -485kV$ ,  $V_2 = -500kV$  and  $I = 1.5kA$
- c)  $V_1 = 500kV$ ,  $V_2 = 485kV$  and  $I = -1.5kA$
- d)  $V_1 = -500kV$ ,  $V_2 = -485kV$  and  $I = -1.5kA$